

A Study of Some Flawed Adders

***** Work In Progress *****

**Robert S. Boyer
and
Warren A. Hunt, Jr.**


Department of Computer Sciences
1 University Station, M/S C0500
The University of Texas
Austin, TX 78712-0233

E-mail: {boyer,hunt}@cs.utexas.edu
TEL: +1 512 471 9745, +1 512 471 9748
FAX: +1 512 471 8885

Circuit Specification, Abstraction, and Reverse Engineering

- Does a manufactured circuit meet its specification?
 - Requires some kind of reverse engineering,
 - Low-level (maybe, transistor-level) analysis,
 - Higher-level specifications, and
 - Verification tools.
- When an ASIC is made ready for manufacturing,
 - technology mapping occurs,
 - synthesis and re-timing are performed,
 - test logic is added, and
 - a floorplan and layout is created.
- Subtle changes can be introduced by foundries.
 - Some circuits are added for testability, reliability, etc.
 - But, are some circuits added as Trojan horses?
- Given a transistor- or gate-level model, could we separate good changes from bad changes?
 - I started to wonder if the number of differences could be measured.
 - I wondered if the number of differences mattered.
 - And, I wondered if measured differences indicated anything.

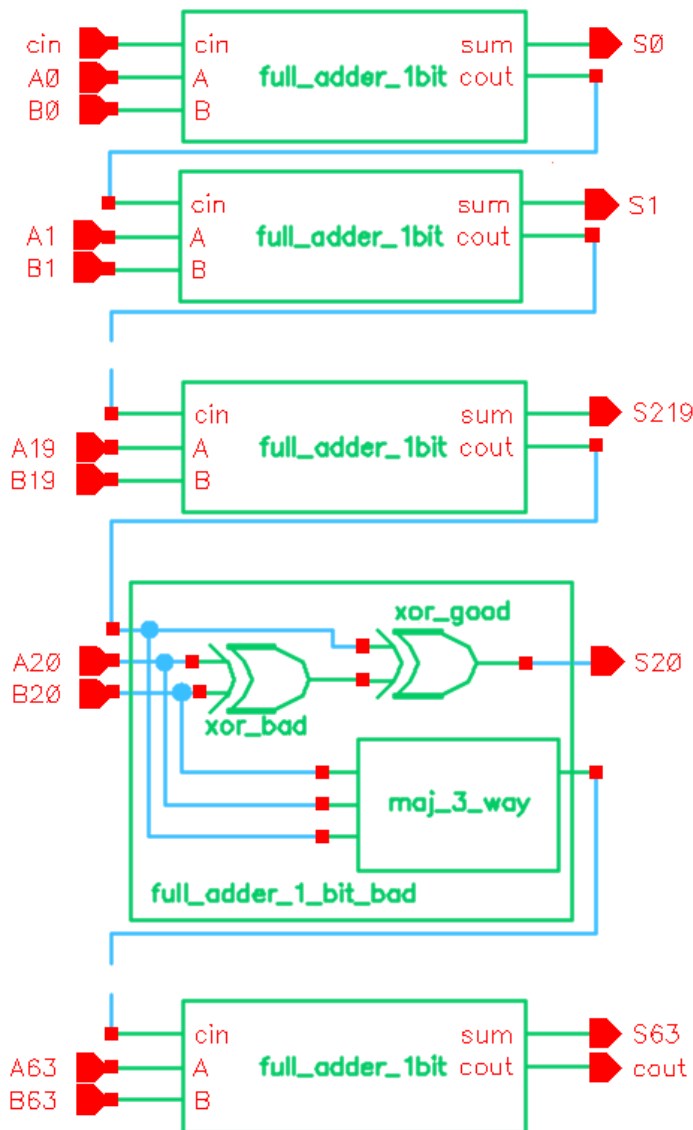Motivating Example: Verification of a Hardware Adder



- It should be easy to verify an adder:
 - adders have a regular structure
 - it just computes a sum.
- However, implementation flaws may still exist:
 - CAD or manufacturing flaws, or
 - Malicious changes might be made.
- To thoroughly verify an adder implementation requires:
 - netlist with transistor strengths, capacitance of wires, etc.
 - a transistor-level analyzer, and
 - a symbolic verifier.
- Could we detect a subtle change?

Circuit Verification and Measured Differences


- Generally, circuits are verified by simulation.
- We advocate symbolic verification, but even so, there may be differences that are acceptable:
 - circuits are used in a restricted environment,
 - circuits used with limited input values, or
 - approximate answers adequate
- Let's count the differences between an XOR and an OR gate.

A	B		OR	XOR	Same	Different
0	0		0	0	1	0
0	1		1	1	1	0
1	0		1	1	1	0
1	1		1	0	0	1

Total:					3	1

Function Representation using BDDs

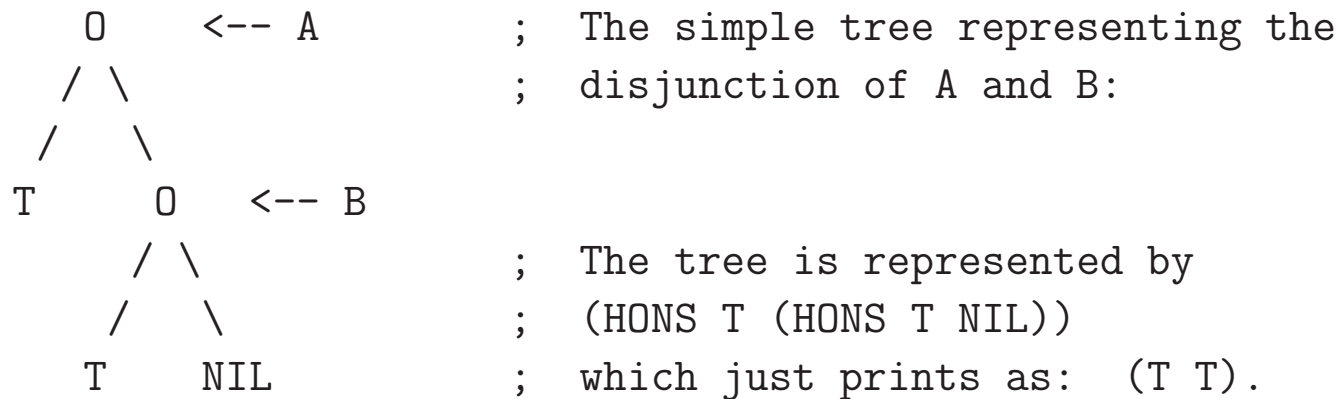- We represent binary functions as HONS trees.
 - The variable order is implicit.
 - The BDDs are reduced – they may terminate early.



- We have defined functions to perform logical operations on BDDs.

<pre> (let* ((a (hons T NIL)) (b (hons a a))) (q-fn 'or a b)) ==> (T T) </pre>	<pre> 0 / \ / \ / \ T NIL </pre>	<pre> 0 / \ / \ / \ B 0 </pre>
-------------------------------------------------------------------------------------------	------------------------------------------------------------------	----------------------------------------------------------------

- Printing large BDDs isn't possible – too much output.

Counting when a BDD Function is 1 or 0

Given a BDD, can we count the number of times the output is 1 and 0?

```
(defun count-tip-values (x depth)
  (if (atom x)
      (mv (if x (expt 2 depth) 0)
          (if x 0 (expt 2 depth)))

      (mv-let
         (left-cnt-1s left-cnt-0s)
         (count-tip-values (car x)
                           (1- depth))

         (mv-let
            (right-cnt-1s right-cnt-0s)
            (count-tip-values (cdr x)
                              (1- depth))

            (mv (+ left-cnt-1s right-cnt-1s)
                (+ left-cnt-0s right-cnt-0s))))))
```

Using COUNT-TIP-VALUES determine the number of input combinations that produce 1 and 0 outputs.

```
(count-tip-values '(t t) 2) ==> (3 1)
```

Let's now produce the *difference* function between the XOR and OR functions.

```
(let* ((a (hons t nil))
       (b (hons a a)))
  (q-fn 'eqv
        (q-fn 'xor a b)
        (q-fn 'or a b)))
```

Using COUNT-TIP-VALUES, we count the differences.

- The second argument provides a bias.

```
(let* ((a (hons t nil))
       (b (hons a a)))
  (count-tip-values
   (q-fn 'eqv
         (q-fn 'xor a b)
         (q-fn 'or a b))
   2))
==>
(3 1)
```

Counting the Difference Between Two Vector of BDD Functions

When counting the differences between two, bit vectors, we compute the maximum number differences.

```
(defun count-max-tip-errors
  (x depth cnt)

  (if (atom x)
      cnt
      (mv-let
        (ones zeros)
        (count-tip-values (car x) depth)
        (declare (ignore ones))

        (count-max-tip-errors
          (cdr x) depth
          (max zeros cnt))))))
```

And when we compare a family of bit vectors to a single, specification bit vector, we compute the smallest, non-zero number of differences.


To determine the differences between two bit vectors, we compute the differences on a bit-by-bit basis.

```
(defun qv-ite-cmp (a b)
  (if (atom a)
      (if (atom b)
          nil
          (cons nil
                 (qv-ite-cmp nil (cdr b))))
      (if (atom b)
          (cons nil
                 (qv-ite-cmp (cdr a) nil))
          (cons
            (q-fn 'eqv (car a) (car b))
            (qv-ite-cmp (cdr a) (cdr b))))))
```

Incomparable positions of bit vectors of uneven length are assigned the maximum number of differences; i.e., NIL.


- We then measure the differences.

Example, Bit Vector Differences

 

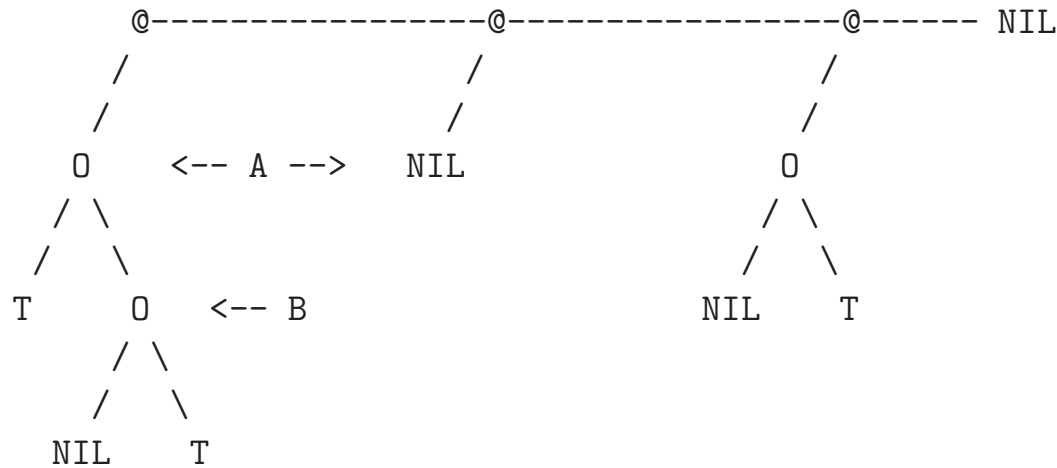Example, Count the Bit Vector Differences


Given the difference equations, the number of differences is shown:



For this result, there are four differences.

When we compare the counts of many bit vectors, we *drop* bit vectors that match.

Single Gate Failures

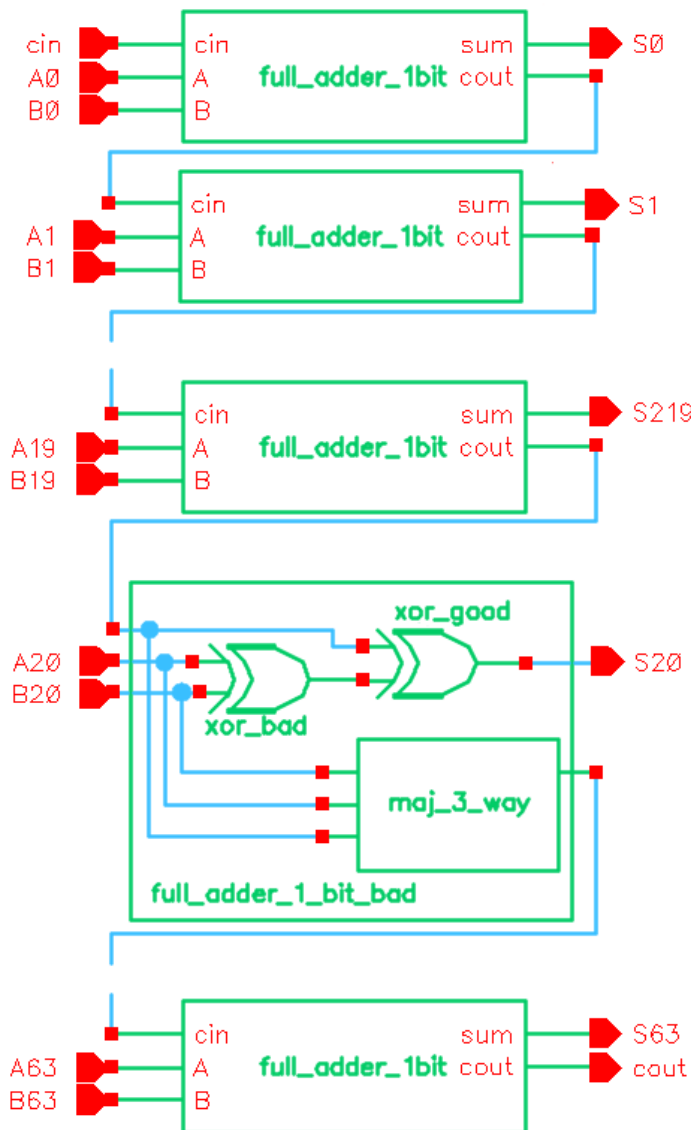

- First Experiment – 64 bit adder.
 - Fault each two-input gate with the other 15 Boolean logic functions.
 - Measure differences.
- There are 4800 flawed adders:
 - 64 bit positions
 - 5 gates per bit position
 - 15 faulty gates per gate
 - 65 equations, 312,000 differences
- Results (for 129 Boolean inputs)
 - For one gate, replacing XOR by OR makes no difference
 - In all other cases we at least find 2^{126} differences in some bit.

Single Input-Pair Failure

Consider a 64-bit adder that returns an incorrect answer for a single pair of numbers.

- Seems like this should be easy to detect by structural means, but
 - Not if exists in purchased IP,
 - Not if embedded in an ALU, or
 - Not if a fabrication change.
- So, we use the developed machinery.

```
(defun sbv-bv-adder
  (c a b a-val b-val ans-val)
  (let
    ((bv-adder (q-bv-adder c a b))
     (cmp-a-val (q-ite-cmp a a-val))
     (cmp-b-val (q-ite-cmp b b-val)))
    (qv-if-ite
     (q-fn 'and cmp-a-val cmp-b-val)
     ans-val bv-adder)))
```

Let's try our subtly flawed adder model. This adder has a built-in key.

```
(v-to-nat
 (sbv-bv-adder
  nil
  (nat-to-v 7 64) (nat-to-v 3 64)
  (nat-to-v 3 64) (nat-to-v 7 64)
  (nat-to-v 11 65)))
==> 10
```

In this case, it works fine, but...

```
(v-to-nat
 (sbv-bv-adder
  nil
  (nat-to-v 3 64) (nat-to-v 7 64)
  (nat-to-v 3 64) (nat-to-v 7 64)
  (nat-to-v 11 65)))
==> 11
```

We can use our counting mechanisms to determine the number of differences.

Count the Bit Vector Differences For Slightly Bad Adder

Given the difference equations, the number of differences is shown:

```
(count-tip-values-list
 (qv-ite-cmp *q-bv-adder* *sbv-bv-adder*)
 (len *all-vars*) 0)
==>
((:CORRECT-ANSWERS 680564733841876926926749214863536422911 :WRONG-ANSWERS 1)
 (:CORRECT-ANSWERS 680564733841876926926749214863536422912 :WRONG-ANSWERS 0)
 (:CORRECT-ANSWERS 680564733841876926926749214863536422912 :WRONG-ANSWERS 0)
 (:CORRECT-ANSWERS 680564733841876926926749214863536422912 :WRONG-ANSWERS 0)
 (:CORRECT-ANSWERS 680564733841876926926749214863536422912 :WRONG-ANSWERS 0)
 ...)
```

We can compute this answer in a few milliseconds.

But, so what?

- Is this a good test for a Trojan Horse type of flaw?
- What other tests might be tried?
- What happens on other functions?

Cone-of-Influence For Slightly Bad Adder

Using the same flawed adder specification, we can compute the cone-of-influence of the inputs for each output.

- For a good adder, the first output bit is dependant on only the input carry and the first bit of the two vectors to be added.
- For our flawed adder, every output is dependent on every input bit.
- Thus, we are investigating the *signatures* of different logic functions using these and other measuring functions.

Discussion

Using unique Boolean function representations and function memoization, we can compute the signatures of thousands of different functions in seconds.

- We actually use a one-argument counting function – it memoizes much more effectively.
- Is this capability just a novelty? Or, could it be useful?
- We find these capabilities useful for bug hunting.